



# Boost your 1500 V string inverter

## Flying-capacitor boost topology for unrivaled cost and performance

---

*Matthias Tauer, Technical Marketing Manager*




*Vincotech GmbH, Unterhaching*

### **Introduction**

This article investigates performance and cost of different boost topologies for 1500 V multistring solar inverters. Designers are seeking for higher level of integration, which means the mounting of the boost inductors on the printed circuit board (PCB). Beside this fact, also efficiency and cost are important aspects to be considered. This case study investigates the optimal solution to meet both requirements at the same time. It introduces a new three-level boost topology named flying-capacitor boost and shows that this topology outperforms in cost and performance.

### **Comparison of boost topologies**

Three different types of boost topologies will be compared: two-level, three-level symmetric and three-level flying-capacitor circuit.

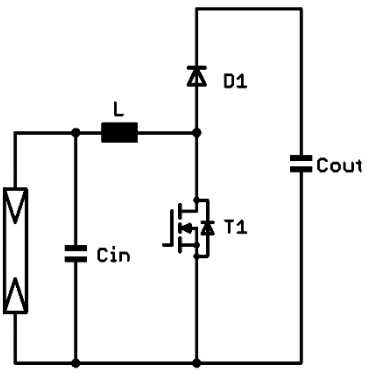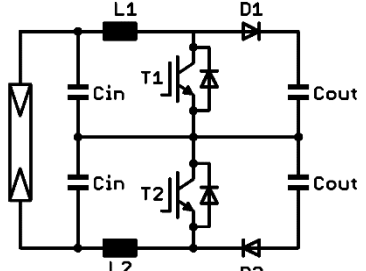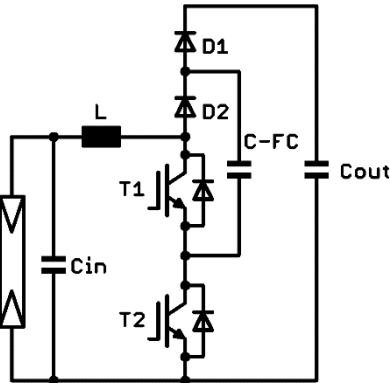two-level boost circuit	three-level symmetric boost circuit	three-level flying-capacitor boost circuit
 <p data-bbox="167 884 470 907">Figure 1: Two-level boost circuit</p>	 <p data-bbox="606 840 973 907">Figure 2: Three-level symmetric boost circuit</p>	 <p data-bbox="1045 840 1460 907">Figure 3: Three-level flying-capacitor boost circuit</p>

The three-level topologies comprise an additional third voltage level. This third voltage level reduces the voltage across the boost inductor, boost switch and diode to half the value required for two-level topologies. Less voltage across the boost inductor has the advantage that the required inductance for a given ripple current is only half of the required inductance at two-level. In consequence the overall inductor volume, weight and cost is reduced. This benefit is not considered in the following power module cost benchmark and should therefore be kept in mind.

In the symmetric boost topology the third voltage level is created by splitting the boost circuit into a positive and negative part. Input and output capacitors are split as well and connected to the neutral point, which provides the additional third voltage level. The pulse-width modulation (PWM) pattern needs to be corrected in order to ensure a symmetry of the neutral point.

The flying-capacitor boost topology creates the third voltage level – as the name indicates – by a floating or flying-capacitor (C-FC). The flying-capacitor shall be charged to half of the output voltage. It is noticeable that only one boost inductor is required.

### Cost and performance benchmark


In this case study the cost and performance is compared for a 21 kW boost leg of a 1500 V multistring solar inverter. Following topologies and chipsets are benchmarked:



chipset	two-level	three-level symmetric	three-level flying-capacitor
Si/SiC hybrid	not examined as efficiency doesn't meet the requirement	1200 V fast Si IGBT 1200 V SiC diode	
full SiC	1700 V SiC MOSFET 1700 V SiC diode	1200 V SiC MOSFET 1200 V SiC diode	

From the efficiency benchmark in Figure 4 it can be seen that the full SiC two-level boost stage has the lowest efficiency (red dotted line) and the highest price (Figure 5). The hybrid chipset would even have lower efficiency in this frequency range and therefore is not taken into account.

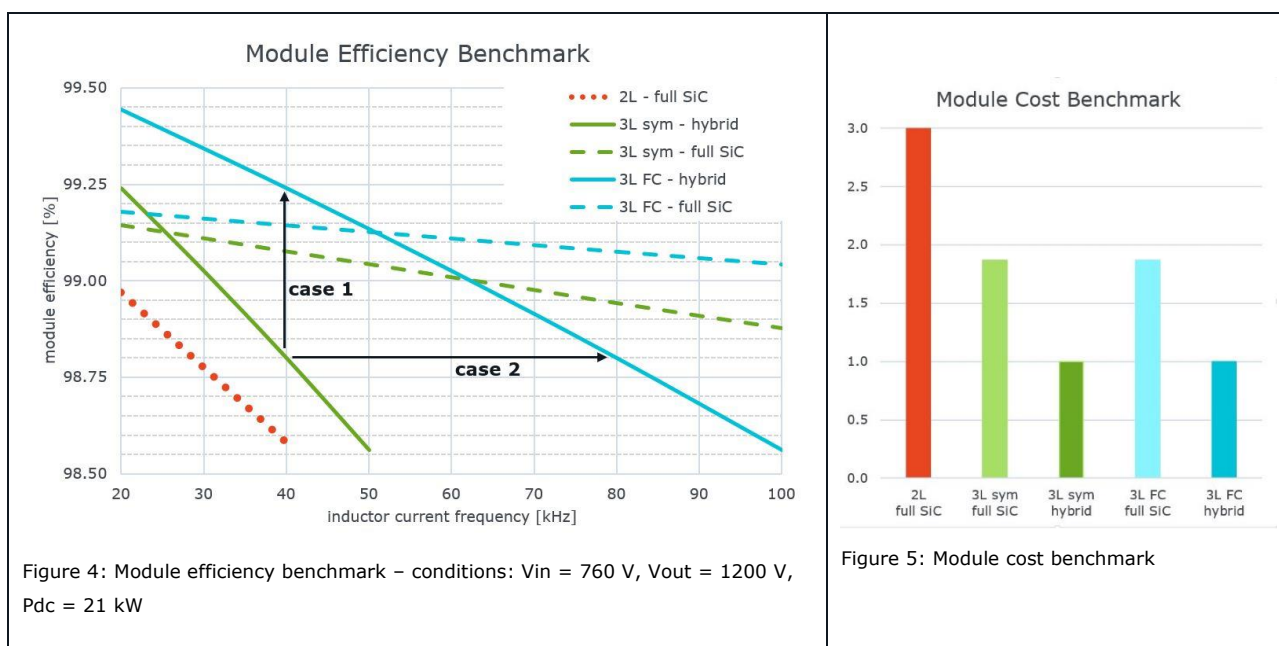The flying-capacitor (FC) boost topology (solid and dashed blue line) shows always higher efficiency as the symmetric boost (solid and dashed green line). Both use the same components and therefore have the same module price. The first conclusion to be drawn is that the flying-capacitor topology has best price and performance ratio compared to symmetric and two-level boost topology.



Up to 50 kHz the hybrid flying-capacitor topology (solid blue line) has the highest efficiency. Above 50 kHz the full SiC flying-capacitor boost circuit (dashed blue line) has the highest efficiency, but also higher price than the hybrid circuit.

The two-level boost and three-level symmetric boost topologies are already well described in the literature and considered as state of the art. In the following section the flying-capacitor topology is discussed.

### Flying-capacitor boost topology in details

The two semiconductor switches T1 and T2 in the flying-capacitor topology are controlled on phase opposition (180° phase shift), but with identical on time (duty cycle). During normal operation T1 and T2 are never turned on at the same time. In continuous conduction mode (CCM) the duty cycle (D) can be calculated to

$$D = 1 - \frac{V_{in}}{V_{out}}$$

The operation is divided into three modes. In mode 1 the low-side switch T2 is turned on and the inductor current is rising. The current is flowing through D2, the flying-capacitor (C-FC) and T2. Once T2 is turned off mode 2 is entered. In mode 2 the current is free-wheeling through D1, D2 and the output capacitor. In mode 3 the floating switch T1 is turned on and the inductor current is rising again. The current is flowing through T1, the flying-capacitor and D1. After turning off T1, mode 2 is entered again and the sequence starts from the beginning. The normal operation mode sequence is: 1 → 2 → 3 → 2 → 1.

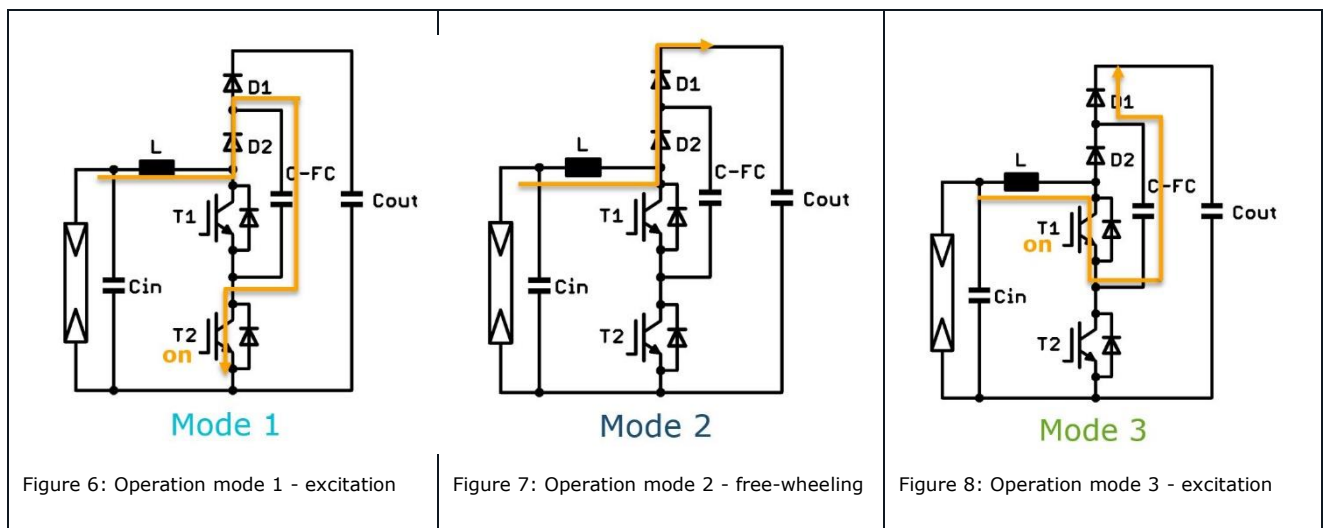


Figure 9 shows for the sake of clarity the gate signals of T1 and T2 together with the boost inductor current  $I_L$ . The inductor current period is defined from one rising slope to the next rising slope. The period of the PWM fundamental switching frequency is defined from the rising edge of T1 or T2 to the next rising edge of the same gate signal. It then shows that the inductor current period is half of the PWM period or in other words the inductor current frequency is double of the PWM frequency.

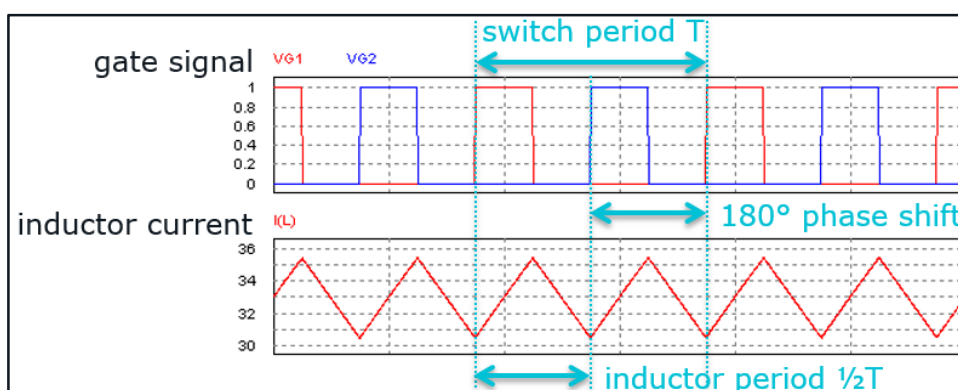


Figure 9: Gate signals of T1 (VG1), T2 (VG2) and boost inductor current I(L)

The flying-capacitor boost topology allows for an existing choke design with fixed inductivity and ripple current to halve the PWM frequency (case 1 in Figure 10). In the first approximation this will also half the semiconductor switching losses and increase the power module efficiency. Figure 4 illustrates case 1 for 40 kHz inductor current frequency: The efficiency can be increased from 98.8% (symmetric boost stage) to 99.24% (flying-capacitor boost stage).

Another potential for optimization is to keep the power module losses constant (same module efficiency), but increase the inductor current frequency (case 2 in Figure 10). Figure 4 shows for case 2 that the efficiency is not changing when the inductor current frequency is doubled from 40 kHz (symmetric boost stage) to 80 kHz (flying-capacitor boost stage).

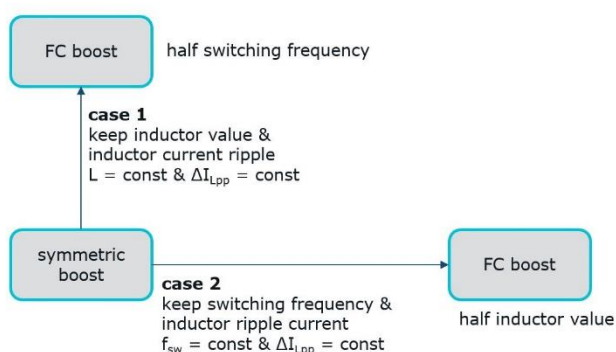


Figure 10

An investigation of the required boost inductance shows that moving from two-level to three-level cuts the inductance to half and the additional doubling of the inductor current frequency further halves the required inductance for the same ripple current.

Boost inductance of two-level can be calculated to



$$L_{2L} = \frac{u_L \cdot t_{on}}{\Delta I}$$

$L_{2L}$ : boost inductance of two-level boost  
 $u_L$ : voltage across boost inductor  
 $t_{on}$ : boost switch on-time  
 $\Delta I$ : inductor current ripple

Moving from two-level to three-level will reduce the voltage across the inductor to half value:

$$L_{3Lsym} = \frac{\left(\frac{1}{2}u_L\right) \cdot t_{on}}{\Delta I} = \frac{1}{2}L_{2L}$$

$L_{3Lsym}$ : boost inductance of three-level symmetric boost  
 $L_{2L}$ : boost inductance of two-level boost

Moving from symmetric boost to flying-capacitor boost topology will double the inductor frequency or half the on-time:

$$L_{3L-FC} = \frac{\left(\frac{1}{2}u_L\right) \cdot \left(\frac{1}{2}t_{on}\right)}{\Delta I} = \frac{1}{2}L_{3Lsym} = \frac{1}{4}L_{2L}$$

$L_{3L-FC}$ : boost inductance of three-level flying-capacitor boost  
 $L_{3Lsym}$ : boost inductance of three-level symmetric boost  
 $L_{2L}$ : boost inductance of two-level boost

## Conclusion and outlook

This article discussed the benefits of flying-capacitor boost topology in regards of cost and performance. The costs for symmetric and flying-capacitor boost topology are the same, but the flying-capacitor boost circuit comprises higher efficiency at the same inductor current frequency. Alternatively, it can even double the inductor current frequency while keeping the module efficiency. In the required frequency range the two-level full SiC boost circuit can't meet the required efficiency and cost.

This article will be continued by taking a closer look into the flying-capacitor topology, discussing its challenges e.g. balancing strategy of the flying-capacitor and further highlighting the system level benefits.

## References

[1] "Symmetrical Boost Concept for Solar Applications up to 1000V", Temesi, Frisch, 01/2009